

INSTRUCTION MANUAL FOR AMPLITUDE MODULATION & DEMODULATION

Amplitude modulation & demodulation apparatus has been designed to study the following:

- A. Amplitude Modulation & Calculation of Modulation Index Percentage Modulation of Side Band Frequency.
- B. Amplitude Demodulator.

The instruments comprises of the following built parts:

1. Fixed output DC regulated power supply of ± 12 Volts.
2. Built in Carrier Sine Wave generator of 450 KHz frequency 2.5V peak to peak amplitude.
3. Built in Audio Frequency Function Generator of 1 KHz 1.5V peak to Peak Amplitude.
4. Circuit diagram for modulator & demodulator are printed on the front panel and components are soldered behind the front panel.

THEORY

Modulation is the process in which some property of high frequency wave, also called as carrier wave ω_c , is altered in such way by low frequency information signal, called as modulating wave ω_m , to transmit from one place to other place through air. In double sideband amplitude modulation the amplitude of carrier wave is altered by modulating wave such to form an envelope upon the carrier on both sides. A non linear element is used to perform the high level modulation and a linear element for low level modulation. Properly biased transistors provide linear/non linear operation with some amplification. The AM wave is represents as shown in fig. (3) and its sidebands as shown in Fig. (4). The top envelope is represents as

$$V_c + V_m \sin \omega_m t,$$

Where the bottom envelope is represented as

$$(V_c - V_m \sin \omega_m t,)$$

When V_c is the carrier voltage, V_m is the modulating voltage. It is shown that formatting of envelopes depends upon the term $V_c + V_m$, where V_c is kept constant hence the envelope height depends upon V_m only. The ratio between envelope amplitude is called as modulation index or factor m_f , which is represented as

$$\frac{V_{max} - V_{min}}{V_{max} + V_{min}}$$


Calculating mf with 100 gives percentage modulation m%, which should never > 100. The power radiated in a given load is related in two terms, one the carrier power Pc and the other is modulated carrier power Pm. The difference of two sideband power Ps which is equal to Pusb+Plsb. The Pm is related with Pc as

$$\frac{P_m}{P_c} = 1 + \frac{mf^2}{2}$$

THEORY OF OPERATION

For Amplitude Modulation

Figure (1) that shows the shows the internal circuit of the chip. We see that the carrier signal is applied to pins 8 and 10 in a common mode to a set of cross coupled differential amplifiers (Q1 with Q4 and Q2 with Q3). Transistor Q7 and Q8 serve as the constant current generator for the differential amplifiers, whereas the bias voltage applied to pin 5 determines the amount of current through the

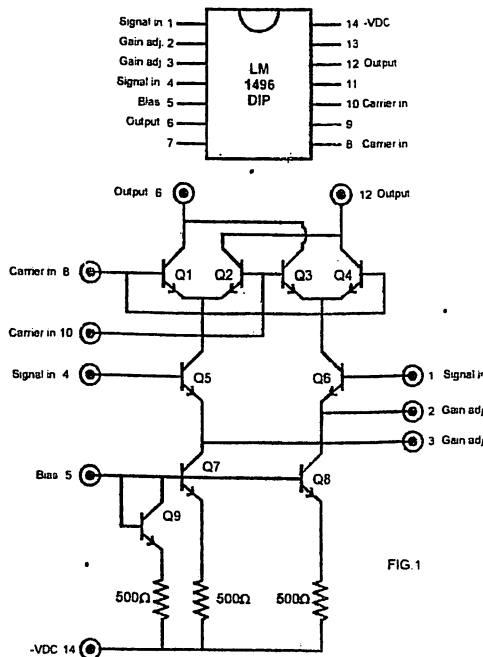

amplifiers. The resistor connected to pins 2 and 3 sets the modulator gain with a smaller resistor resulting in higher gain. The DC voltage difference between pins 1 and 4 will balance the differential amplifiers for complete carrier rejection by equalizing the current in each differential amplifier. When the message signal is applied to pins 1 and 4 transistor Q5 and Q6 will alternately increase (or decrease)

the current through their associated amplifier to output the sum and difference frequencies in the side band pair. The output is taken pin 6 for the modulator.

DEMODULATION OF AM WAVE

There are many procedures to demodulate the amplitude modulated waves. In present board (envelope detection) linear diode demodulation circuitry is provided. In linear diode detector circuits, diode presents a low ohmic path to input signal in

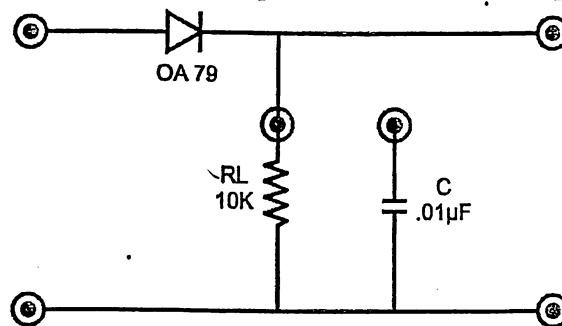


FIG.2

one direction only. For this reason changes in the peak current through the diode will remain confined to straight portion of Volt-ampere characteristics of the diode in other words it can be said that it acts as half wave rectifier carrier wave components. When carrier is presented only the average current I_{avg} will pass through the diode and has a constant amplitude output. When modulated wave is at the input the current I_{peak} varies through forms a low pass filter to remove these HF components (in actual practice pe filters are employed). The maximum time constant is kept $\max RLC = 1/\omega_c \omega_m$.

The detection efficiency of diode detector is calculated from the input modulated signal power, or by mean of modulation depth and detected output as

$$\beta = \text{average potential across } RL / \text{peak input signal voltage}$$

The maximum detection efficiency lies between 80-90%, and upto 60-70% of modulation index.

PROCEDURE

For Modulation

1. Connect the carrier OSC output to carrier input.
2. Connect AF signal output to AF signal input.
3. Connect CRO channel A with the Amplitude Modulation output sockets.
4. Connect the CRO channel B with the AF signal output sockets.
5. Keep the Amplitude control at minimum position.
6. Switch ON the instrument using ON/OFF toggle switch.

7. Adjust CRO time base for 0.2ms/DV and vert gain at 1V/Div a band will appear upon the screen. Position it at the center of the screen & calculate

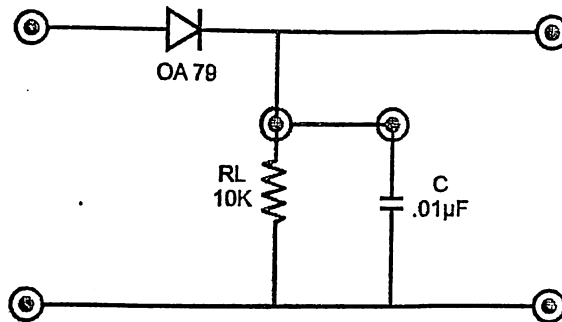


FIG.3

the value of modulation index percentage modulation upper side band frequency and lower side band frequency.


Formula used calculation of modulation index or modulation coefficient and side band frequencies.

$$m_a = \frac{2V_{\max} - 2V_{\min}}{2V_{\max} + 2V_{\min}}$$

$$\text{Percent modulation} = m_a \times 100\%$$

Upper side band frequency = carrier signal frequency + modulating signal frequency.

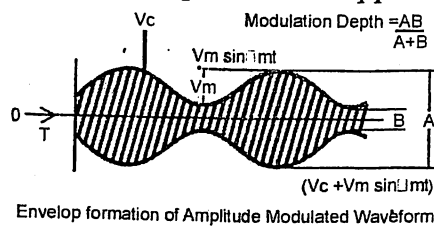8. Connect the resistance box across the modulated output sockets in parallel with CRO leads measure the signal in Vpp.
9. Feed one volt p-p AF signal to the AF input. Trace out the pattern of the modulated wave and measure amplitudes in Vpp as shown in Fig. (4).



Envelop formation of Amplitude Modulated Waveform

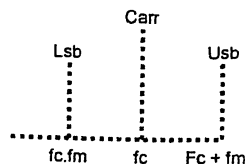


Fig.4


10. Increase AF input to successive levels and note amplitude A and B, for each increment. Calculate modulation factor for each input. Draw a plot between input signal (AF) modulation factor. The curve of the graph shown the modulation process. Increase maximum AF signal to observe the distorted wave form since cut-off and saturation of the transistor Q5.

11. Calculate peak power and $P_c = V_{PP}^2 / R_L$ and modulated power $2P_m = V_A^2 / R_L$, where V_A is the pp amplitude traces from modulated envelope. Find out the power in side bands as p side bands = P_m . PC.
12. Plot side bands spectrum measuring AF and carrier signal frequencies.
13. Trigger CRO with input signal (For external triggering)

Note: - If resistance box and resistor is not available then modulated output may be terminated in provided $R_L = 10K$ in demodulator circuit as shown Fig. (3) & Fig. (4).

For Demodulation

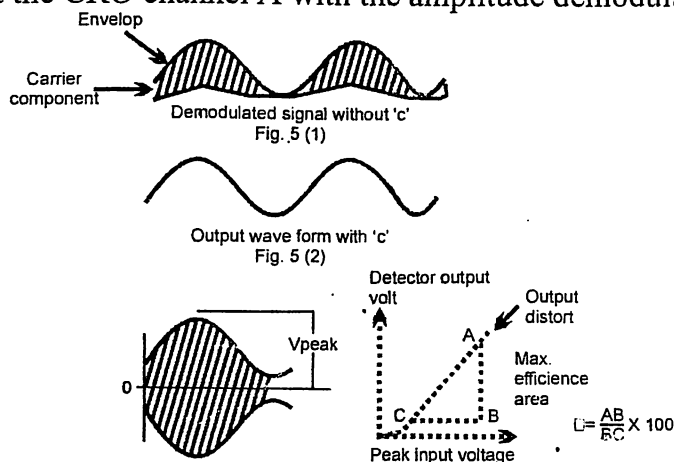1. Connect the Amplitude modulation circuit to the input of Amplitude demodulation circuit.
2. Connect the CRO channel A with the amplitude demodulation output.



Different wave form at demodulator and its response curve
Fig. 5 (3)

3. Remain C out Circuit and no R_L should be connected across modulated output sockets then the output is as shown in fig. 5 (i).
4. Connect CRO channel B with the AF modulated signal output.
5. Connect C in the Circuit and note its effect upon the RF components as shown in Fig. 5 (ii).
6. Feed AF signal for different modulation factor and note the amplitude of demodulated output voltage in p-p, and input voltage as $V_p = V_{pp}/2$ or A/S .
7. Plot a response curve between output voltage and V_p input. Select the linear part of the curve and calculate the efficiency of the detector as $\beta = \text{Slope of the curve}$ as shown in Fig. 5 (iii).

INSTRUCTION MANUAL FOR PUSH-PULL AMPLIFIER



Push-Pull Amplifier Apparatus has been designed to study the Output Gain, Output Power and Frequency Response of a Push Pull Amplifier.

The Instrument comprises of the following built in parts :-

DC Regulated power supply of 12V.


Two L plate (Driver Transformers) matching transformers.

Three NPN transistors (CL100) are mounted on the front panel & important connections brought out on sockets.

Different types of resistances and capacitors are mounted on the front panel.

THEORY

Push Pull Amplifier is a power amplifier and is frequently employed in the output stages of electronic circuits. It is used whenever high output power at high efficiency is required. The circuit diagram shows the circuit of a push pull amplifier. Two transistors TR₁ and TR₂ placed back to back are employed. Both transistors are operated in class B operation i.e collector current is nearly zero in the absence of the signal. The centre tapped secondary of driver transformer T₁ supplies equal and opposite voltage to the base circuit of two transistors. The output transformer T₂ has the centre-tapped primary winding. The supply voltage V_{cc} is connected between the bases and this centre tap. The output load is connected across the secondary of this transformer. Input signal appears across the secondary AB of driver

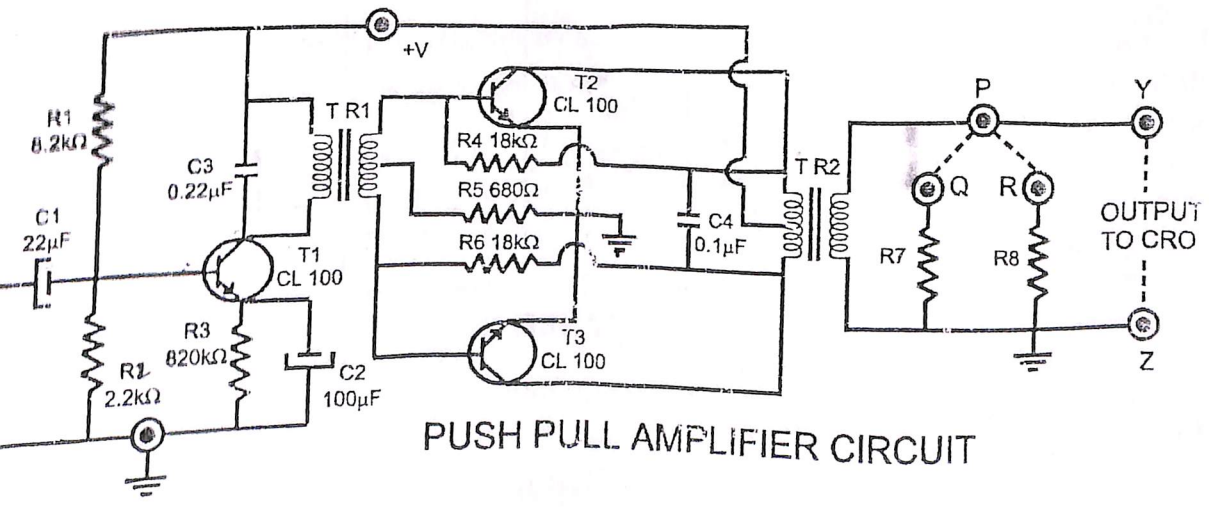

PUSH PULL AMPLIFIER CIRCUIT

...mer. Suppose during the first half cycle of the signal, end A becomes positive and end ...ive. This will make the base emitter junction of TR₁ reverse biased and that of TR₂ ...biased. The circuit will conduct current due to TR₂ only. Therefore, this half cycle of the