

# INSTRUCTION MANUAL

## FOR

### APPLICATIONS OF OPERATIONAL AMPLIFIER KIT

Operational Amplifier Circuits has been designed to study the following :-

1. Operational amplifier as Inverting Amplifier.
2. Operational amplifier as Non-Inverting Amplifier.
3. Operational amplifier as Summing Amplifier.
4. Operational amplifier as Difference Amplifier.
5. Operational amplifier as Differentiator.
6. Operational amplifier as Integrator.
7. Operational amplifier as Sine Wave Generator.
8. Operational amplifier as Sine to Square Wave Convertor.
9. Operational amplifier as Square to Triangular Wave Convertor.
10. Operational amplifier as Unity Gain Amplifier.

### THEORY

The operational amplifier is a versatile device that can be used to amplify dc as well as ac input signals and was originally designed for computing such mathematical functions as addition, subtraction, multiplication, and integration. With the addition of suitable external feedback components, the modern day op-amp can be used for a variety of applications, such as ac and dc signal amplification, active filters, oscillators, comparators, regulators, and others.

An ideal op-amp exhibit the following electrical characteristics :

1. Infinite voltage gain  $A$ .
2. Infinite input resistance  $R_i$  so that almost any signal source can drive it, and there is no loading of the preceding stage.
3. Zero output resistance  $R_o$  so that output can drive an infinite number of other devices.
4. Zero output voltage when output voltage is zero.
5. Infinite bandwidth so that any frequency signal from 0 to Hz can be amplified without attenuation.

Infinite common-mode rejection ratio so that the output common-mode noise voltage is zero.

Infinite slew rate so that output voltage changes occur simultaneously with input voltage changes.

### PROCEDURE

**E:**  $V_+$  (+15V) &  $V_-$  (-15V) power supplies are already connected internally. Only you have to connect the circuit through patchcords.

Operational amplifier as Inverting Amplifier:-

Connect the circuit as shown in fig. no. (1).

Use  $R_1$  (1K $\Omega$ ) in the input circuit and  $R_F$  (10K $\Omega$ ) in the feed back circuit.

Set the input voltage ( $V_{IN}$ ) at 0.5V.

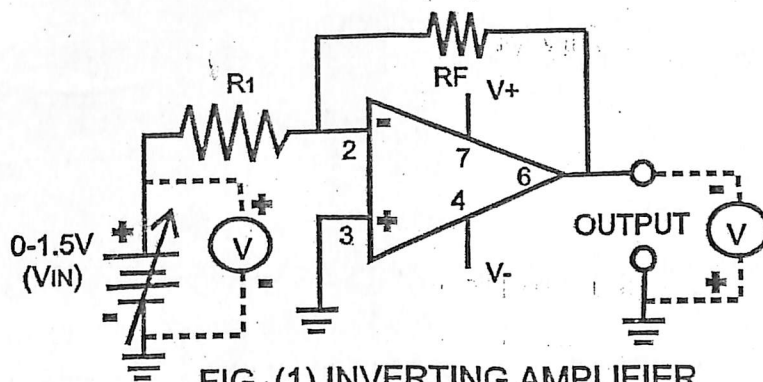


FIG. (1) INVERTING AMPLIFIER

Note down the output using DC voltmeter.

Repeat steps 2 - 4 for different input voltages. (0.75Volt and 1Volts).

Formula for calculation of output voltage:-

$$V_{OUT} = -V_{IN} [R_F / R_1]$$

Operational amplifier as Non Inverting Amplifier :-

Connect the circuit as shown in fig. no. (2).

Select  $R_1$  in the input circuit and  $R_F$  in the feedback circuit.

( $R_1 = 1K\Omega$ ,  $R_F = 10K\Omega$ )

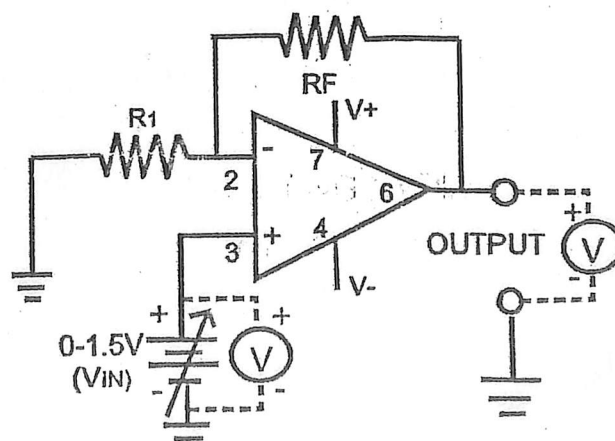


FIG. (2) NON-INVERTING AMPLIFIER

Set the input voltage ( $V_{IN}$ ) at 0.5V

Note down the output using DC Voltmeter.

Repeat steps 2-4 for different input voltages. (0.75V and 1V).

Formula for calculation of output voltage:-

$$V_{OUT} = V_{IN} [1 + R_F / R_1]$$

### Operational amplifier as Summing Amplifier (as Adder) :-

Connect the circuit as shown in fig. no. (3).

Apply input voltages of 1V from both the supplies. Also choose  $R_1$  and  $R_2$  in the input circuit as both are equal to  $10k\Omega$ .

Note down the output voltage.

Repeat steps 2 & 3 for different input voltages keeping  $R_1$  &  $R_2$  as it is.

Calculate the output voltage using formula:-

$$V_{out} = -[V_{IN} (R_F / R_1) + V_{in} (R_F / R_2)]$$

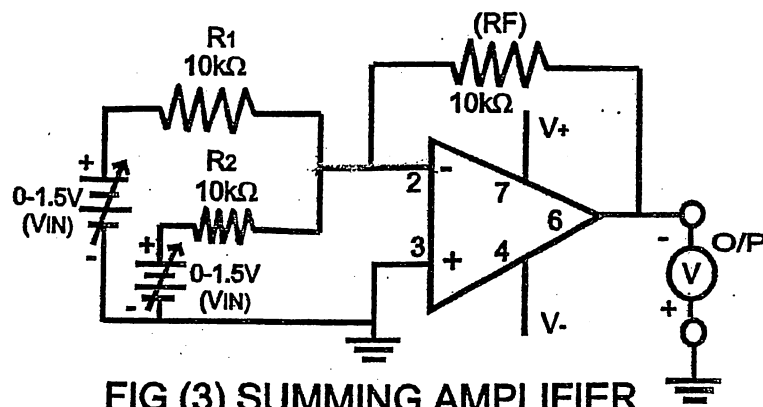


FIG (3) SUMMING AMPLIFIER

### Operational amplifier as Difference Amplifier (As Subtractor) :-

Connect the circuit as shown in fig. no. (4).

Apply input voltage of 0.5V at pin no. 2 and 1.5V at pin no. 3 from both the supplies. Also choose  $R_1$  and  $R_2$  in the input circuit as both are equal to  $10k\Omega$ .

Note down the output voltage.

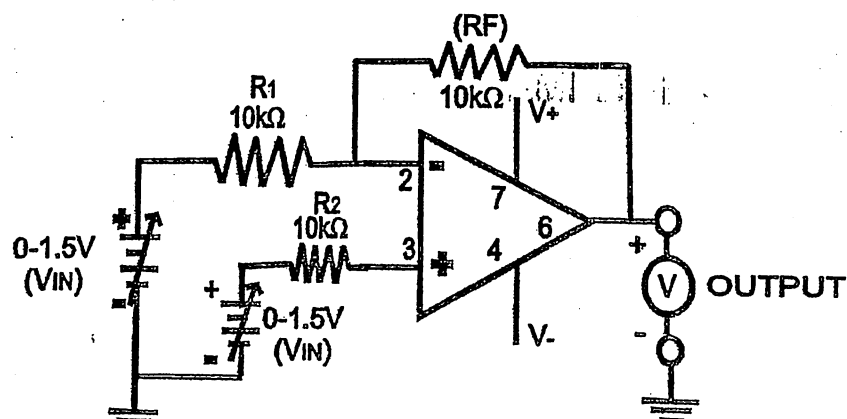


FIG. (4) DIFFERENCE AMPLIFIER

Repeat steps 2 & 3 for different input voltages keeping R & R as it is.

Calculate the output voltage using formula:-


$$V_{out} = V_{in} (1 + R_F/R_2) - V_{in} (R_F/R_1)$$

**E :** Always apply higher voltage at pin no. 3 as compare to pin no. 2.

### Operational Amplifier as Differentiator Circuit:-

Connect the circuit as shown in fig. no. (5).

Use capacitor C<sub>1</sub> (0.1μf) in the input circuit and R<sub>F</sub> (10kΩ) in the feed back circuit.

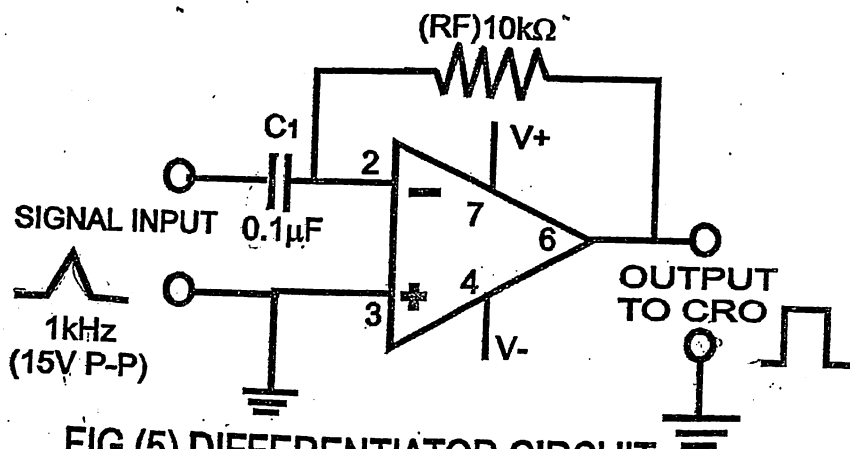

**FIG (5) DIFFERENTIATOR CIRCUIT**

Connect Audio Frequency Function Generator across input of the circuit & CRO across output.

Apply triangular wave of 15 Volts peak to peak amplitude, 1kHz frequency across input.


Observe the output wave form on CRO. It should be a square wave.

### Operational Amplifier as Integrating Circuit :-

Connect the circuit as shown in fig. no. (6).

Use resistance R<sub>1</sub>, R<sub>F</sub> (10kΩ) & C<sub>1</sub> (0.1μF).

Connect Audio Frequency Function Generator across input of the circuit & CRO across output.

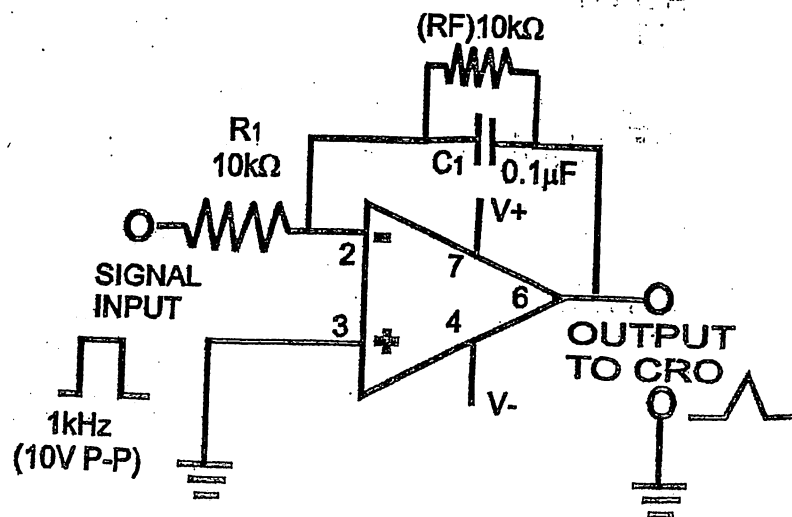

**FIG (6) INTEGRATOR CIRCUIT**

Apply square wave of 10Volts peak to peak amplitude, 1kHz frequency